



T.E. (Electronics and Industrial Electronics) (Semester – II)
Examination, 2009
LINEAR INTEGRATED CIRCUITS
(1997 Course)

Time : 3 Hours

Max. Marks : 100

- Instructions :** 1) Answer *any 3* questions from *each* Section.
2) Answers to the *two* Sections should be written in *separate* books.
3) *Neat* diagrams must be drawn *wherever* necessary.
4) *Black* figures to the *right* indicate *full* marks.
5) Use of logarithmic tables, slide rule, Mollier charts, electronic pocket calculator and steam tables is *allowed*.
6) Assume suitable data, if *necessary*.

SECTION – I

1. a) Discuss with the help of block schematic the principle of operation of PLL.
b) Explain the terms “Lock range” and “Capture range”. State the factors governing these ranges.
c) Draw a circuit of typical “voltage controlled oscillator” and explain its operation. **18**

2. a) For the circuit shown in fig. (a)
 - 1) Find V_0/V_{in} for $V_{in} > 0$
 - 2) Find V_0/V_{in} for $V_{in} < 0$
 - 3) Derive the condition so that V_0/V_{in} is same in both half cycles. **10**

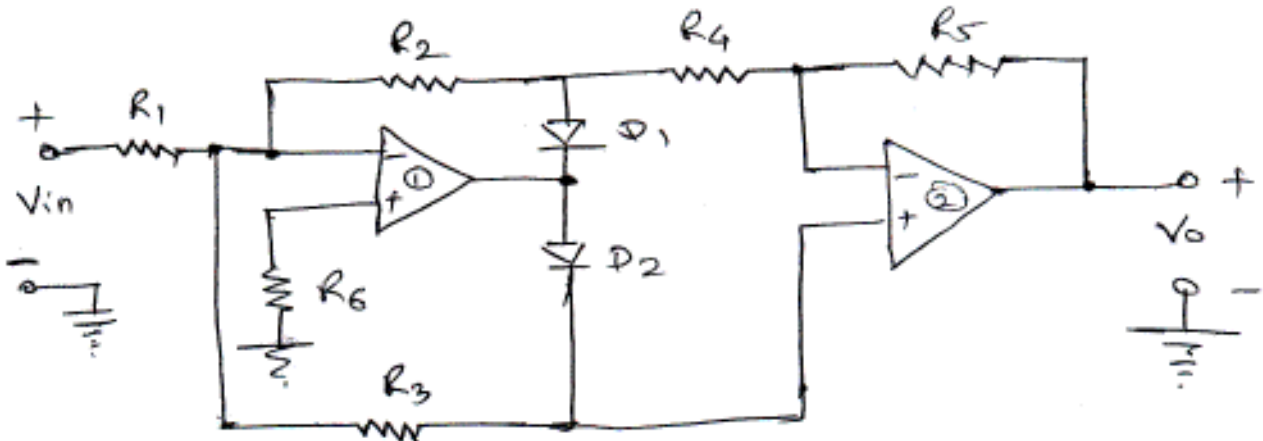


Fig. (a)



b) 1) Describe the function of the circuit shown in fig. (b)

2) Draw the waveforms at various points for positive V_{ref} .

6

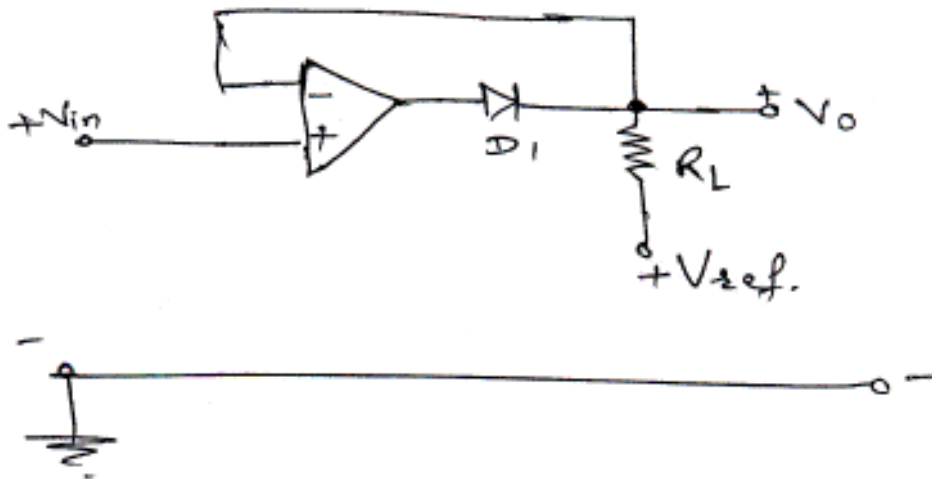


Fig. (b)

3. a) Draw a neat circuit diagram of a peaking amplifier. Label the components properly. Assume that the inductor used has a series resistance R_s .

2

b) Derive the expression for its parallel equivalent resistance R_p .

2

c) Derive the expression for its parallel equivalent inductance L_p .

2

d) Hence derive the expression for the voltage gain $A_v(j\omega)$ of the peaking amplifier.

4

e) Hence derive the expression for the peak voltage gain A_{vo} .

2

f) Find out the Q coil as a function of frequency.

2

g) Find out the Q coil at a peaking frequency.

2

4. a) Explain with internal circuit diagram working of Norton amplifier in inverting mode.

6

b) Design an inverting Norton amplifier for a gain of 12 using LM3900. Use 9v single power supply. Input impedance be $100\text{ k}\Omega$ s. Assume source impedance zero ohms, lower cutoff frequency 100 Hz, and load impedance of $20\text{ k}\Omega$ s.

10



5. Write short notes on (any two) :

16

- a) Programmable gain amplifier
- b) PID controller
- c) Schmitt trigger
- d) Sample and hold circuit.

SECTION – II

6. a) Explain I to V converter with the help of an application for D to A converter.

8

b) Derive an expression for output voltage of a Log-ratio amplifier and explain its working with help of circuit diagram.

8

7. a) Explain the need of linearization of signals from transducers.

Discuss in short any two techniques of linearization.

8

b) What are the sources of common mode noise ? Explain how instrumentation amplifier help to reduce this noise.

8

8. a) Derive the expression for i_L for the circuit shown in fig. (c).

8

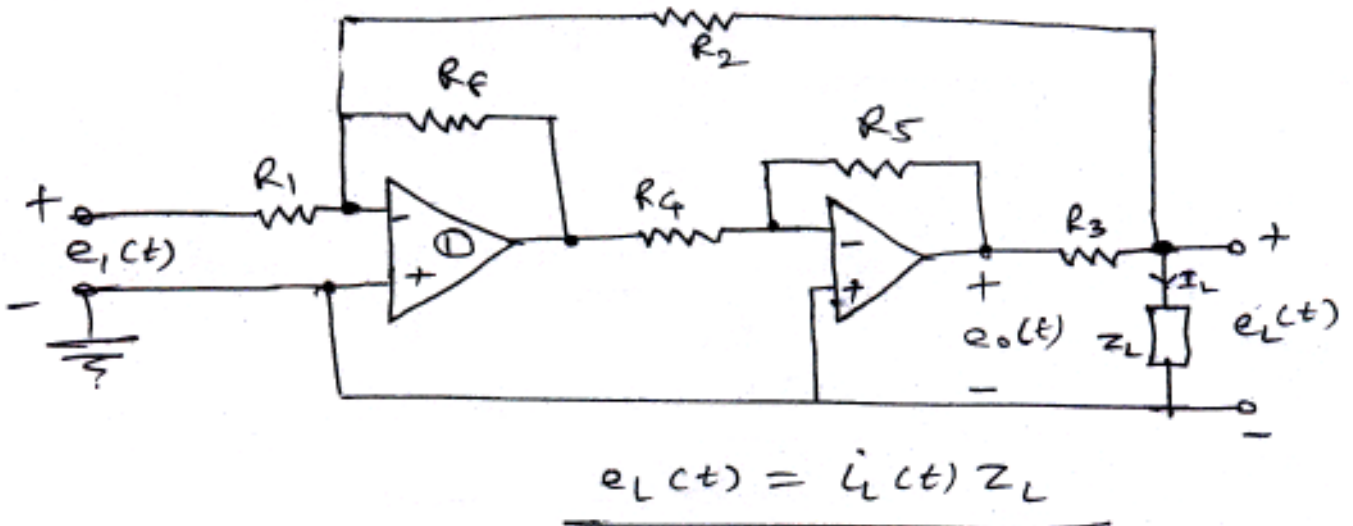


Fig. (c)



- b) With a neat diagram, describe the operation of IC LM 2907 as a frequency to voltage converter. 8

 - 9. a) Using IC 7805 (Three terminal regulator) design a current source to deliver op-amp current to 20Ω , 10 watts load. 8

 - b) What are the advantages of using active loads in op-amp circuits ? 2

 - c) Explain how temperature dependent reverse saturation current gets eliminated by using logarithmic ratio amplifier. 6

 - 10. Write short notes on (**any three**) : 18
 - a) Power amplifier IC
 - b) PLC and FSK demodulator
 - c) Graphic equalizer
 - d) Wein bridge oscillator
 - e) Function generator using ICL 8038.
-



[3563] – 9

**T.E. (Electronics) (Sem. – II) Examination, 2009
NETWORK THEORY
(1997 Course) (Old) (Common to I.E.)**

Time : 3 Hours

Max. Marks : 100

- Instructions :**
- 1) Answer **any 3** questions from **each** Section.
 - 2) Answers to the **two** Sections should be written in **separate** books.
 - 3) **Neat** diagrams must be drawn **wherever** necessary.
 - 4) **Black** figures to the **right** indicate **full** marks.
 - 5) Your answers will be valued as a **whole**.
 - 6) Use of logarithmic tables, slide rule, Mollier charts, electronic pocket calculator and steam tables is **allowed**.
 - 7) Assume suitable data, if **necessary**.

SECTION – I

1. a) Explain following terms with reference to the graph theory.
 - 1) Planar and non-planar graph.
 - 2) Tree and cotree.
 - 3) Incidence matrix.
 - 4) Fundamental cut set matrix.
 - 5) Fundamental loop matrix. 10
- b) Compare time domain analysis with frequency domain analysis. Give advantages of the Laplace transform analysis. 6
2. a) What are even signal and odd signals ? Resolve following signals into even parts and odd parts. 10

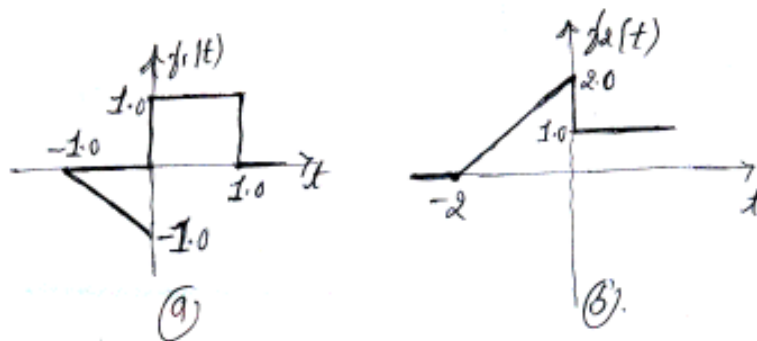


Fig. 1

- b) Give six important properties or theorems on Laplace Transform. 6

P.T.O.



3. a) What are unit impulse, unit step and unit ramp functions ? Establish relationship between them. 6
- b) Find the Laplace Transform of following waveforms shown in Fig. 2. 8

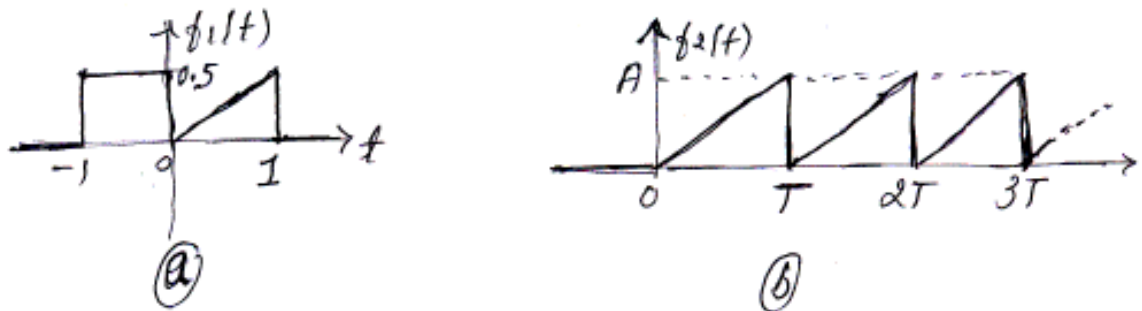


Fig. 2

- c) Find the Inverse Laplace Transform of 4

$$F(s) = \frac{(1 + e^{-3s})}{s^2(s + 2)}$$

4. a) In the R-L circuit shown in Fig. 3 switch was on position 1 for a long time and steady state is reached. At $t = 0$ it is thrown on position 2. Find the resultant current $i_1(t)$ using L.T. method. 8

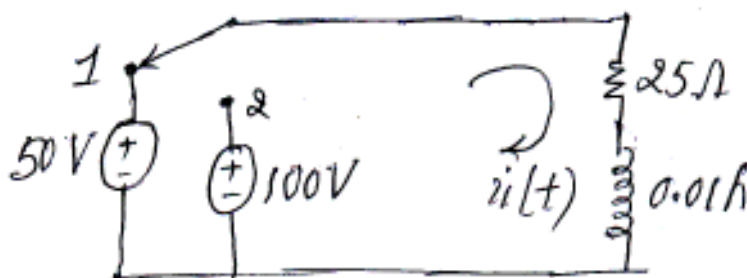


Fig. 3



b) For the network shown find the following network functions.

$$\alpha_{21}(s) = \frac{I_2(s)}{I_1(s)}, \quad G_{21}(s) = \frac{V_2(s)}{V_1(s)}, \quad Z_{21}(s) = \frac{V_2(s)}{I_1(s)}. \quad 8$$

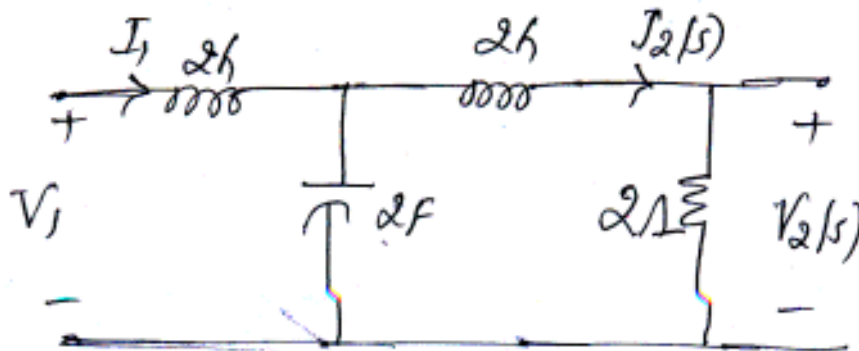


Fig. 4

5. a) Find the residues at the poles of the function using graphical method and then find Inverse Transform. 8

$$F(s) = \frac{(s+2)(s+2)}{s(s^2+4)}$$

b) Write a brief short note on : 8
1) Incidental dissipations
2) Poles and zeros.

SECTION – II

6. a) What are network parameters ? With equations explain Z and T parameters. Obtain T-parameters in terms of Z-parameters. 8



b) Find Z and Y parameters for the circuit shown in Fig. 5.

8

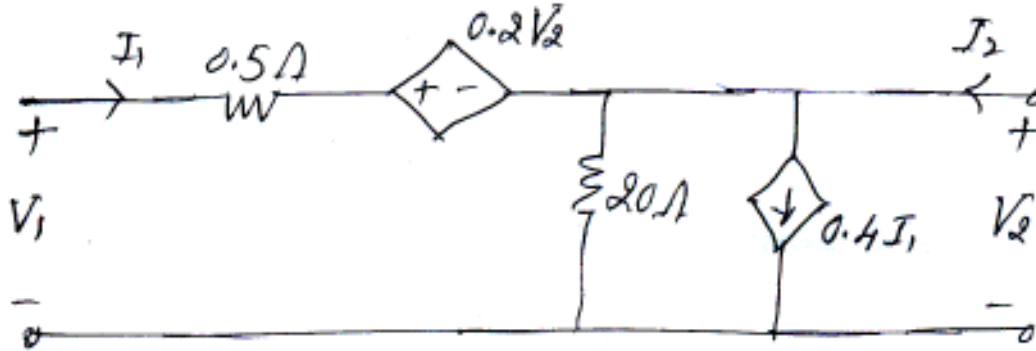


Fig. 5

7. a) Explain necessary and sufficient conditions for a function to be Positive Real function.

4

b) What is Hurwitz polynomial? Test whether following function is Hurwitz.

6

$$P(s) = s^7 + 2s^6 + 2s^5 + s^4 + 4s^3 + 8s^2 + 8s + 4$$

c) Test whether following functions are prf

8

$$1) F_1(s) = \frac{s^2 + 6s + 5}{s^2 + 9s + 14}$$

$$2) F_2(s) = \frac{2s^2 + 2s + 4}{(s+1)(s^2 + 2)}$$

8. a) Give the properties of driving point L-C impedance functions.

4

b) Realize following function into Cauer – I and Cauer – II forms.

8

$$Z(s) = \frac{s^4 + 10s^2 + 9}{s^3 + 4s}$$

c) Realise following function into Foster – II form

4

$$Y(s) = \frac{s(s+2)}{(s+1)(s+4)}$$



9. a) Synthesize following function into L-C ladder network with 1s termination. **6**

$$Z_{21}(s) = \frac{s^3}{s^3 + 3s^2 + 4s + 2}$$

- b) Compare Butterworth and Chebyshev filter approximations. **4**

- c) Design a 1st order B.W. active filter having a passband gain of 20 dB and cutoff frequency of 2 KHz. **6**

10. a) Write short note on : **8**

- 1) Impedance scaling and frequency scaling.
- 2) Gyrator and its applications.

- b) Realize a normalized LP Butterworth filter having following specifications. **8**

- 1) Passband specification of $|H(j0.5)|^2 > 0.9$
- 2) Stop band specification of $|H(j2)|^2 < 0.01$
- 3) $R_s = R_o = 1$ ohm.